



# Potentiostat Design and Engineering


Prepared By:

Sujan Shrestha, PhD

*Applications Engineer*

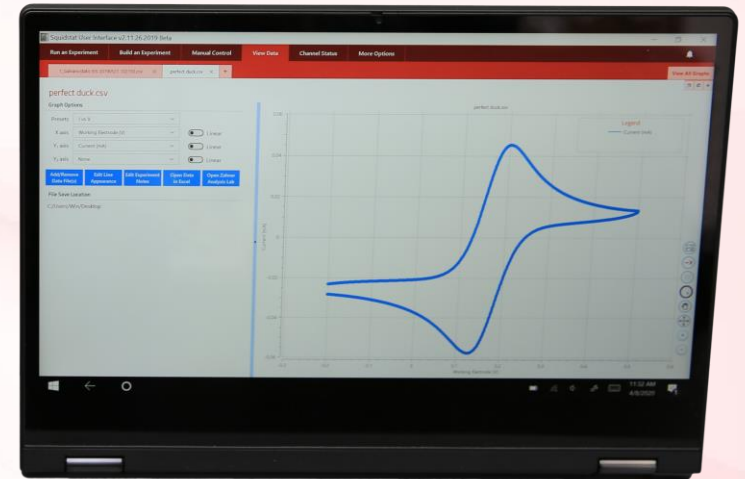
# Topics To Be Discussed

- Potentiostat Functions
- Operational Amplifiers
- Potentiostat Stability
- Current and Voltage Ranges
- Ground/Float Mode



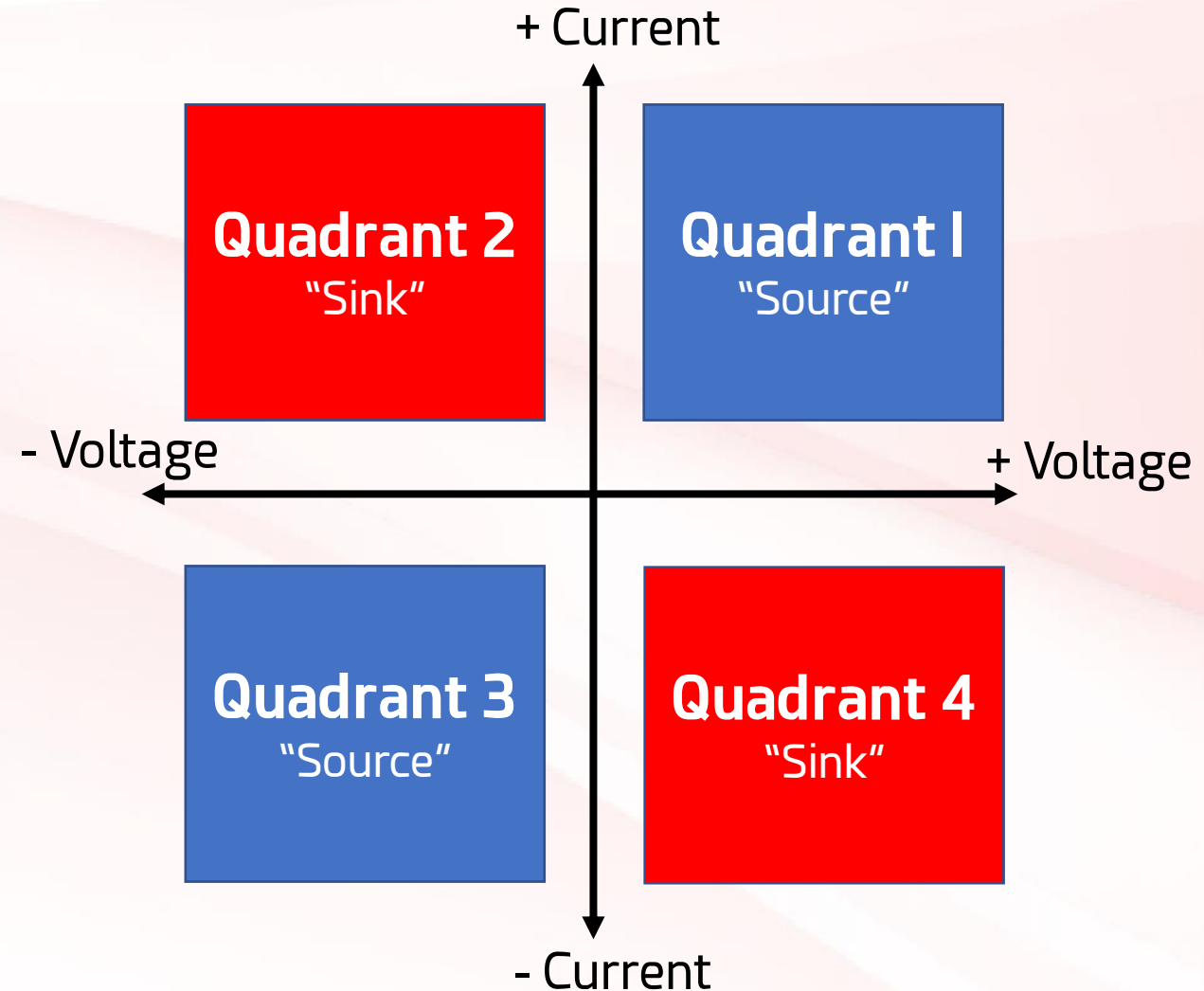
# Different Types of Power Instruments

- Power instruments are designed to source and/or sink power from the device under test
- Conventional power supply operate in Quadrants 1 and/or 3
- Conventional Loads operate in Quadrants 2 and/or 4
- Potentiostats and Source Measurement Units operate in all four quadrants



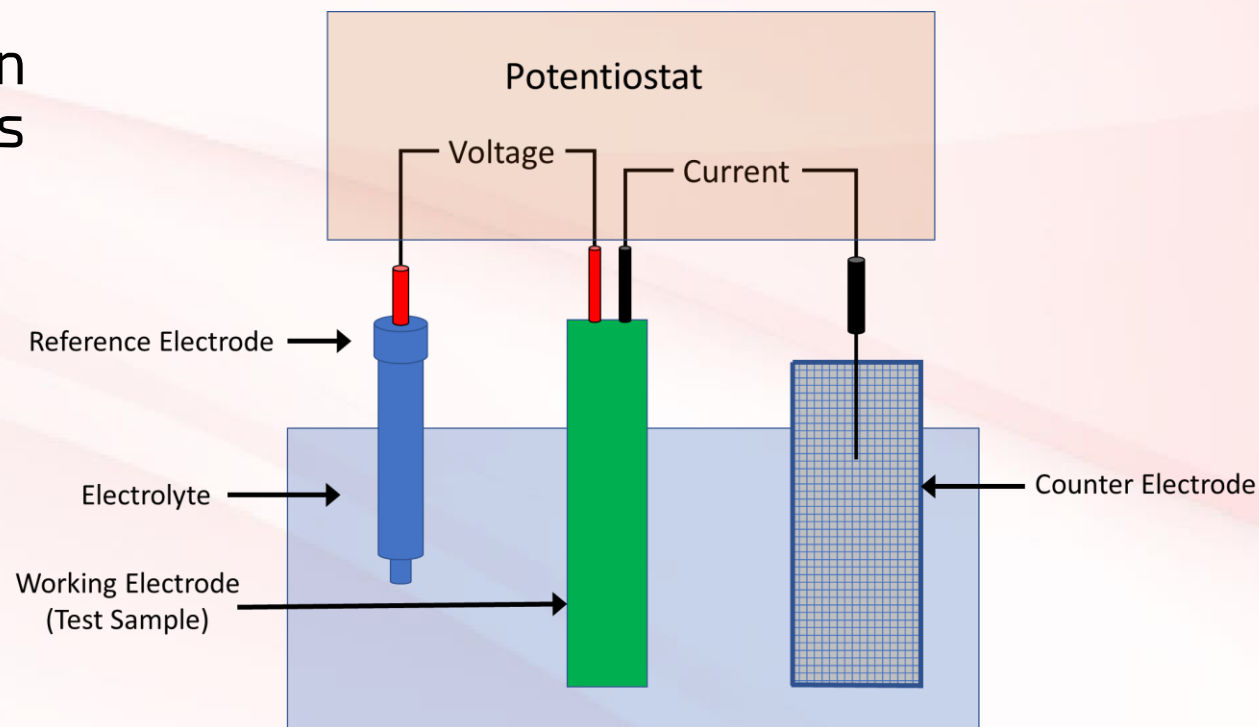
# What is a Potentiostat?

- Runs 3-electrode potentiostatic experiments. Modern potentiostats run in both potentiostat and galvanostat modes
- A set voltage is applied on the Working Electrode (WE) with respect to the Reference Electrode (RE), while current flows between WE and RE
- Current does not flow through the RE
- Counter electrode can be at a different voltage than RE



# Basic Functions of a Potentiostat

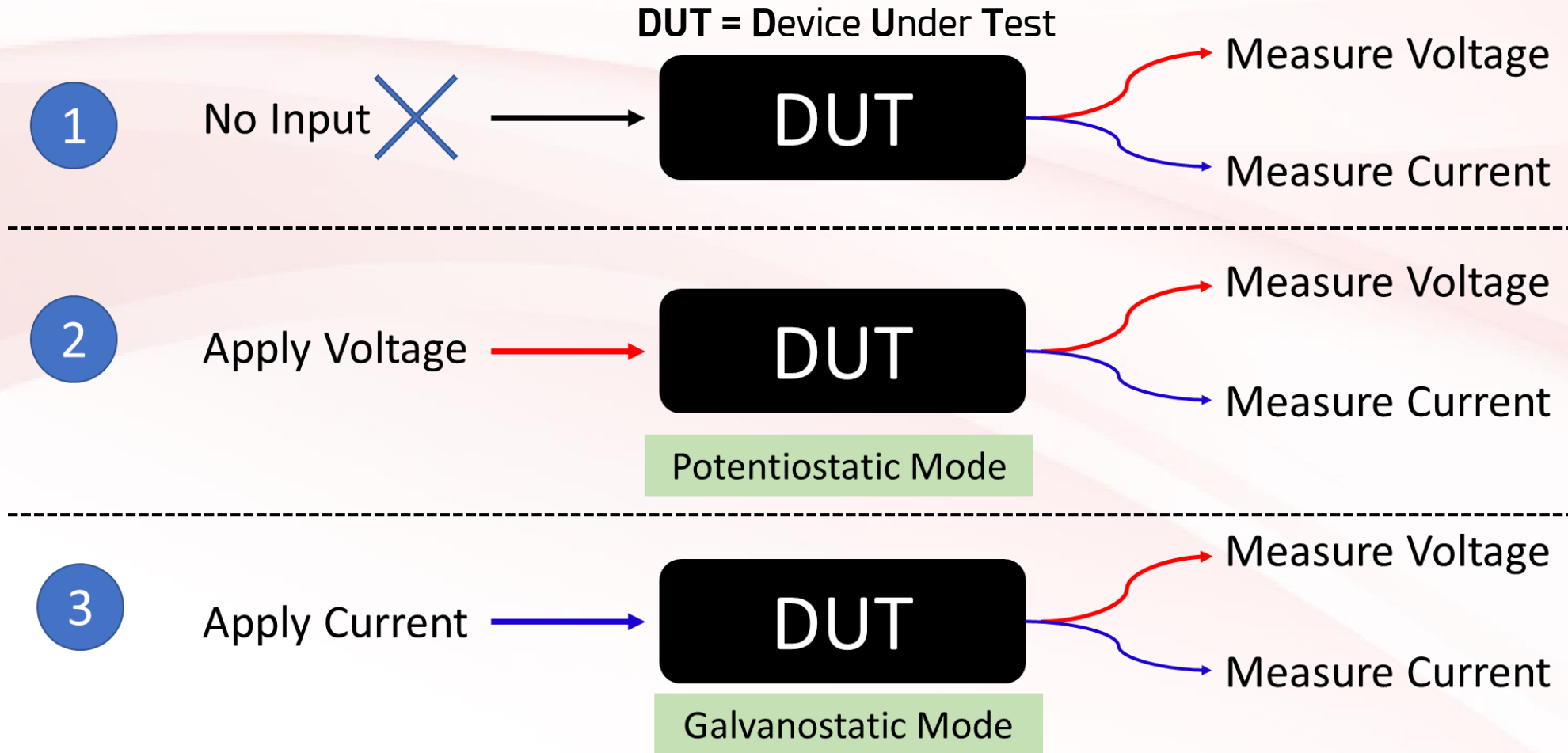


# Varieties of Voltage and Current Signals


**Constant Potential/Current**




**Pulse**

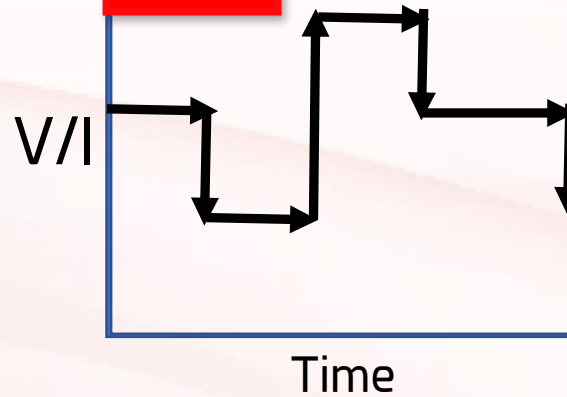

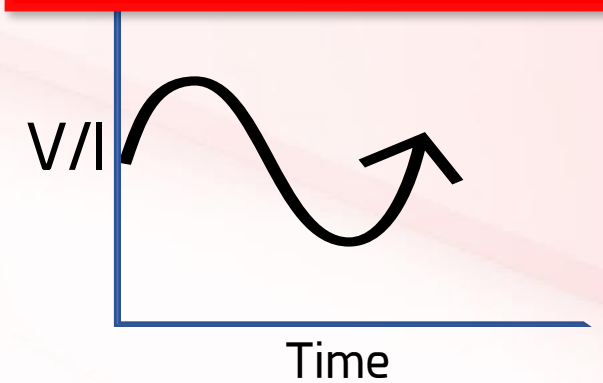
**Electrochemical Impedance Spectroscopy**



**Linear Sweep Voltammetry**

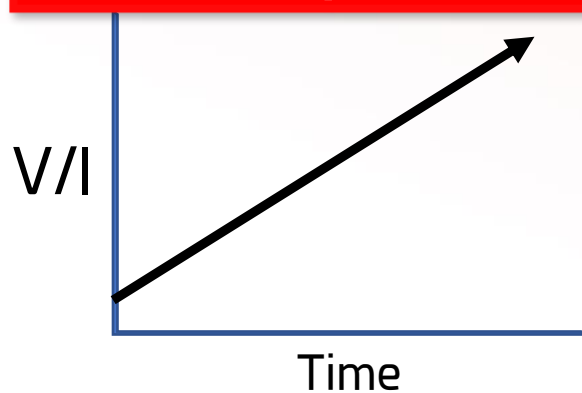


**Cyclic Voltammetry**

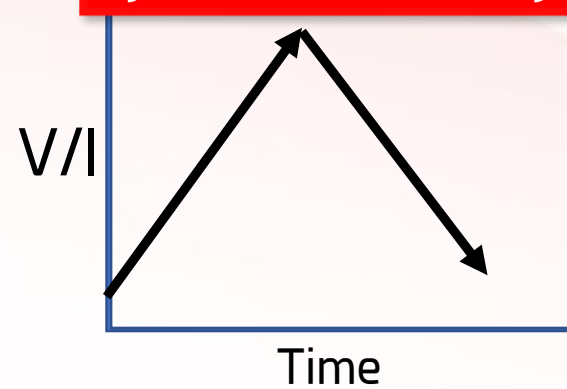





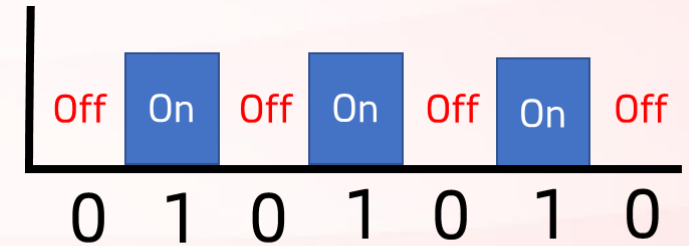
# Digital Nature of Potentiostats


- Signals are sent and received as 0's and 1's



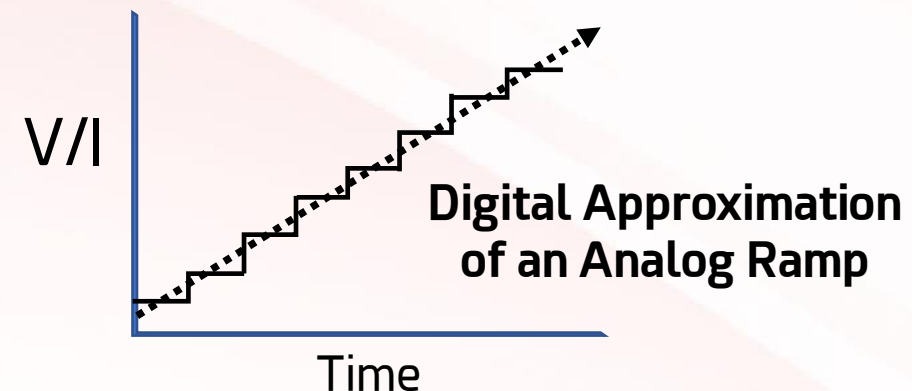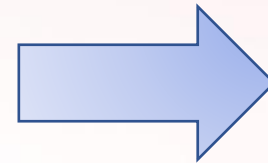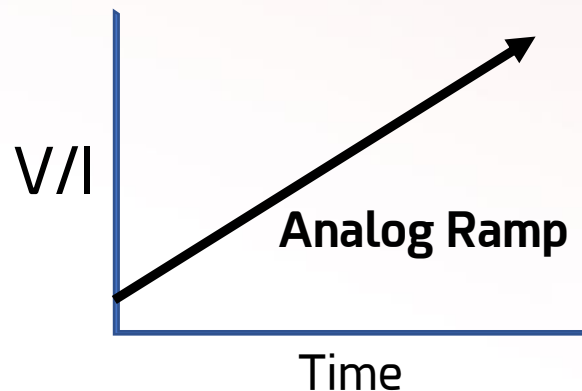- A step signal is the basic building block of all applied and received signal from the device under test



# Basic Potentiostat Architecture

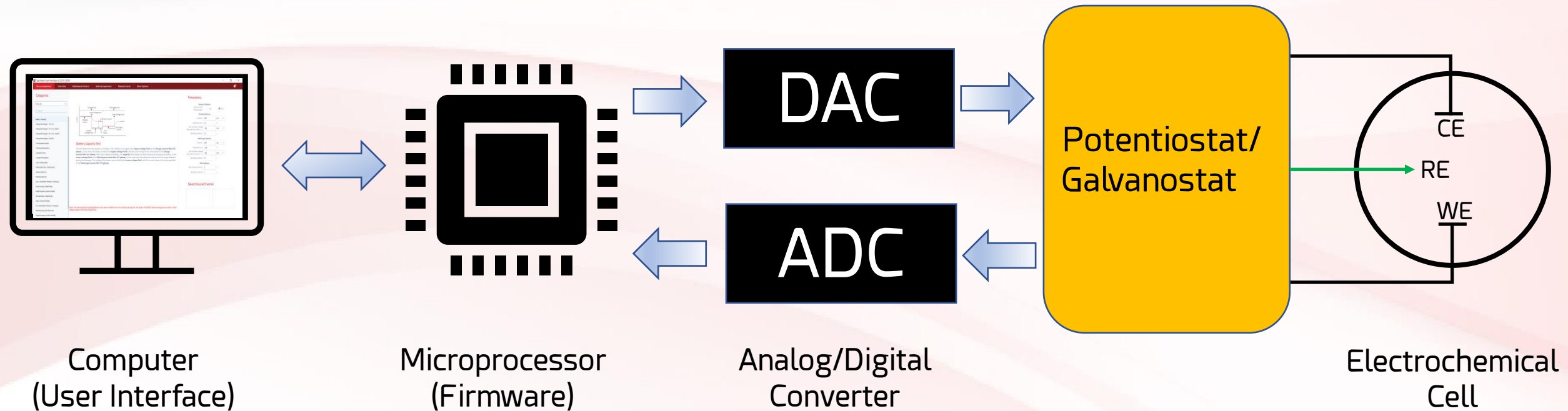


DAC = Digital to Analog Converter  
ADC = Analog to Digital Converter

 Signal Flow Pathway



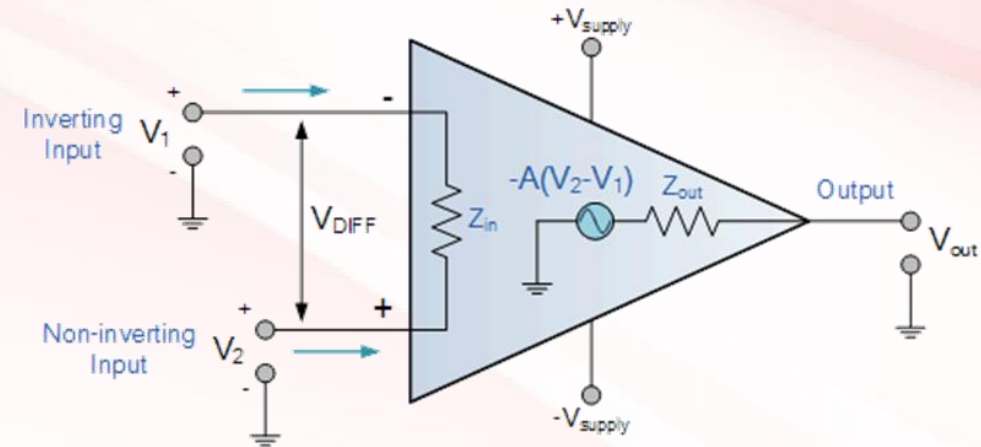
# Ideal Operational Amplifier (Op-amps)

- Operational Amplifier (op-amps)
  - Building blocks of the potentiostat
  - "Operational" - originally used to do math operations
  - "Amplifier" - amplifies the input signal [ $V_{out} = A \times (V_2 - V_1)$ ]
- Characteristics of an ideal op-amp
  - Open-loop gain ( $A_{OL}$ ) = infinity
  - $Z_{in} = \text{infinity}$
  - $Z_{out} = 0$
  - **Response time = zero, infinite bandwidth**
  - Offset = zero ( $V_{out} = 0$  if  $V_2 - V_1 = 0$ )



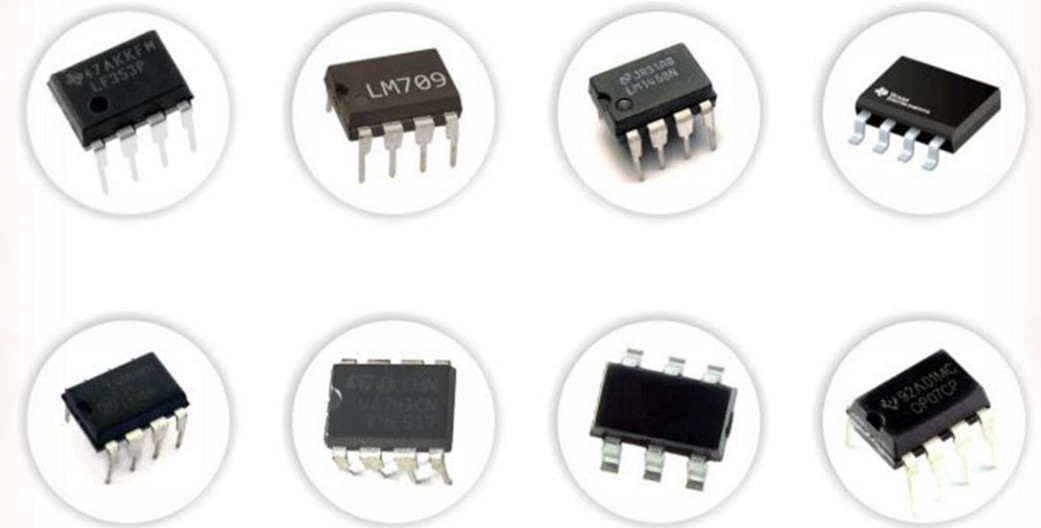
# Operational Amplifier Classifications

- Types based on Current/Voltage input-output
  - Voltage in-Voltage out
  - Current in-Current out
  - Voltage in-Current out (Transconductance)
  - Current in-Voltage out (Transresistance)
- Types based on specifications
  - Universal
  - High resistance
  - Low temperature drift
  - High speed
  - Low power
  - High Voltage High Current
  - Programmable
- Other types
  - Differential
  - Instrumentation


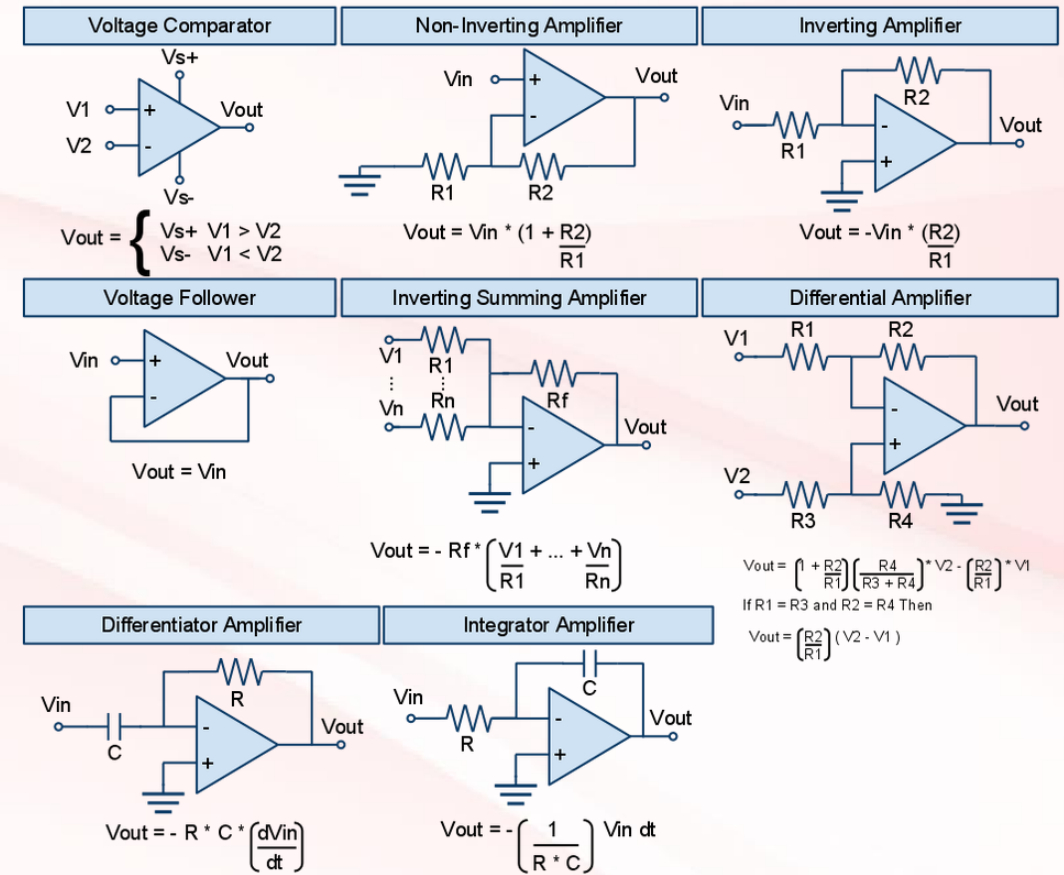
# Some Basic Types of Op-Amps Circuits


- The configuration of op-amps are limitless (logic, mathematic, filter, etc)
- Negative-feedback loop (the output is connected to the inverting input) is the most common configuration
- In fact, an op-amp is rarely used in open-loop (no feedback loop) configuration




**Basic Operational Amplifier Configurations**
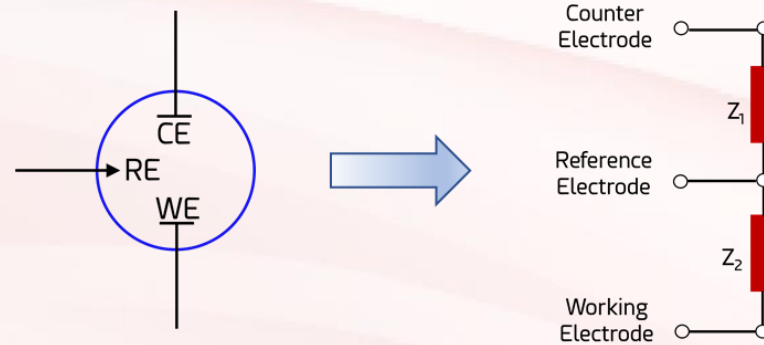
# Making Potentiostats Using Op-Amps



- An electrochemical cell can be simulated with resistors and capacitors



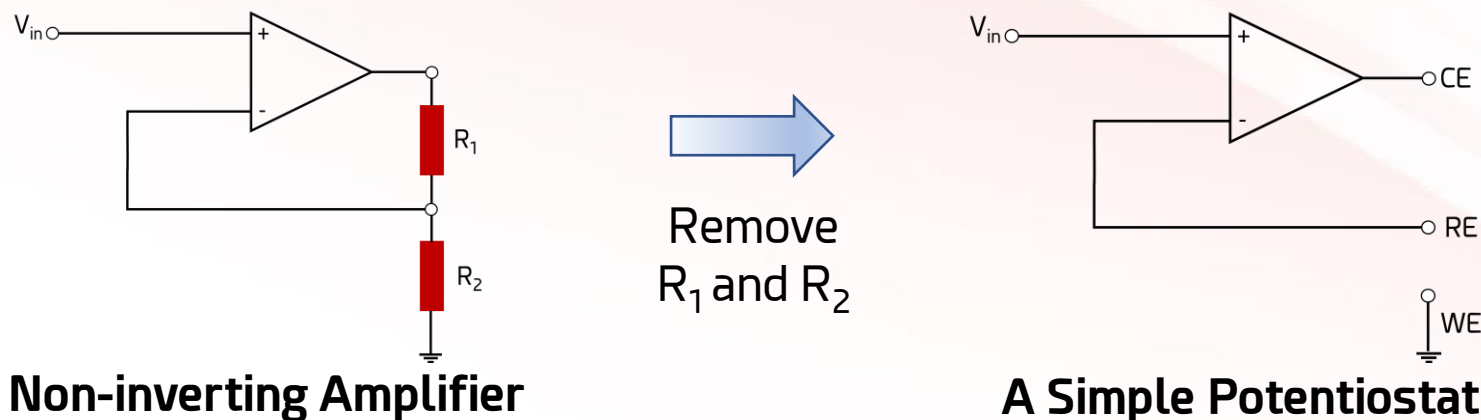- A simple potentiostat can be created using one of the basic op-amp circuits




# A Real Potentiostat is Complex!

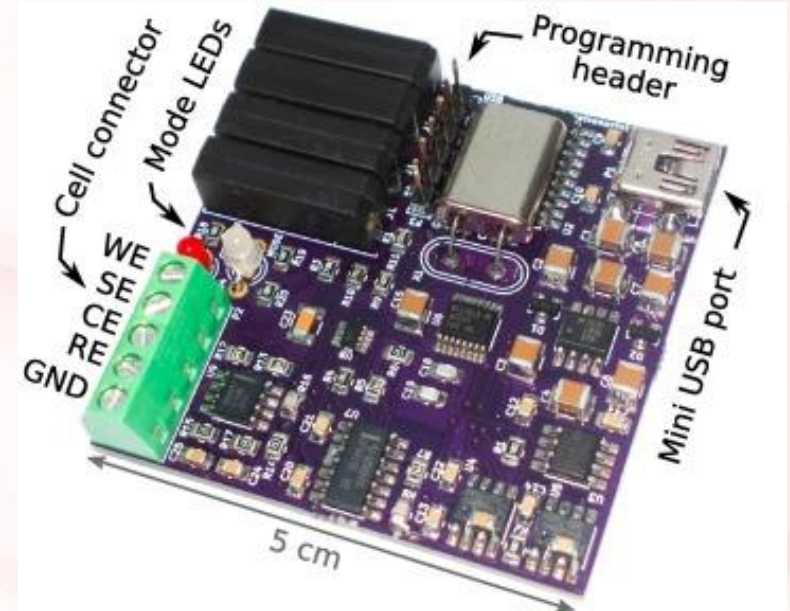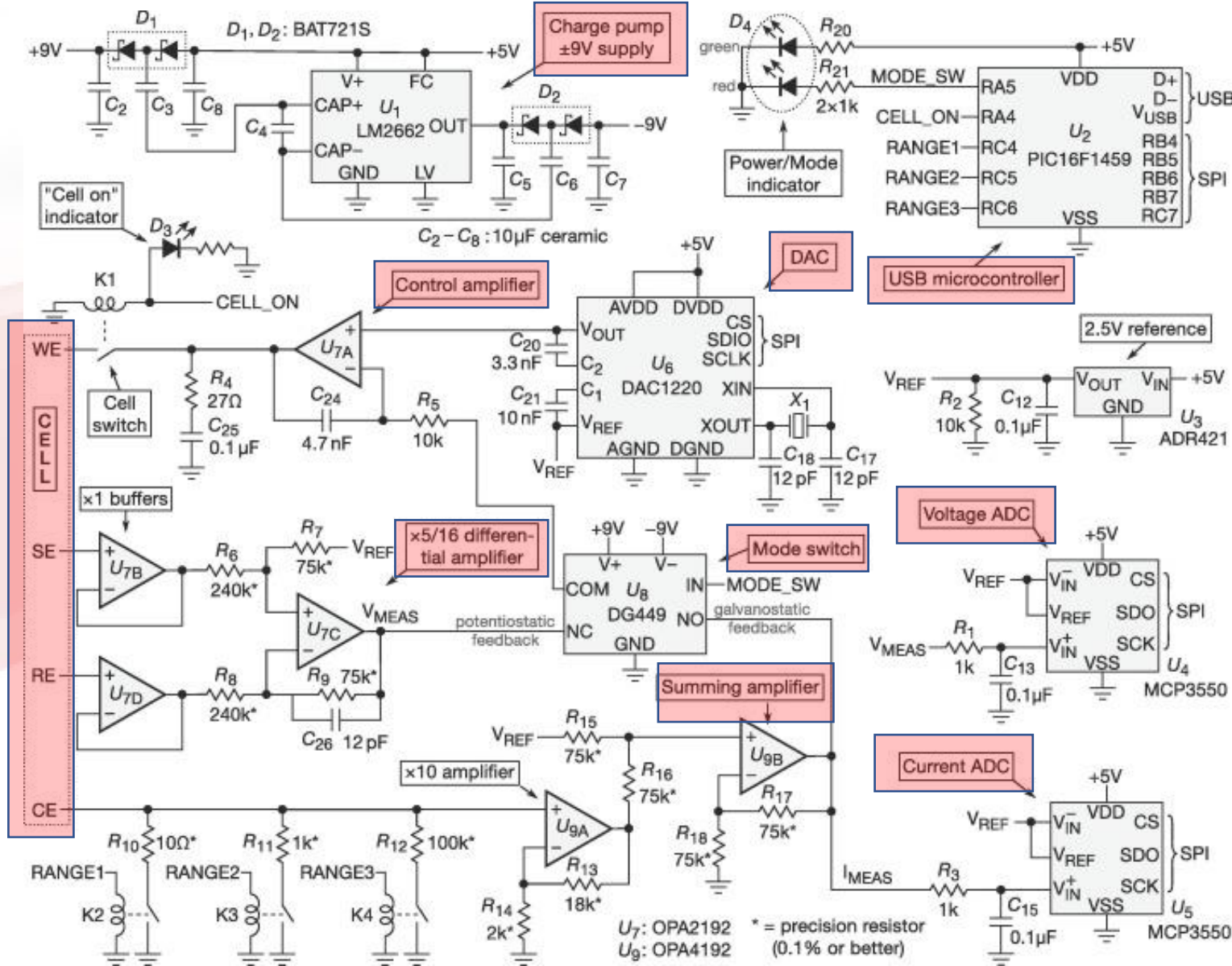

*"A USB-controlled potentiostat/galvanostat for thin-film battery characterization"*  
 Dobbelaere, et al. Hardware X 2 (2017) 34-49




# Simplified Potentiostat Design

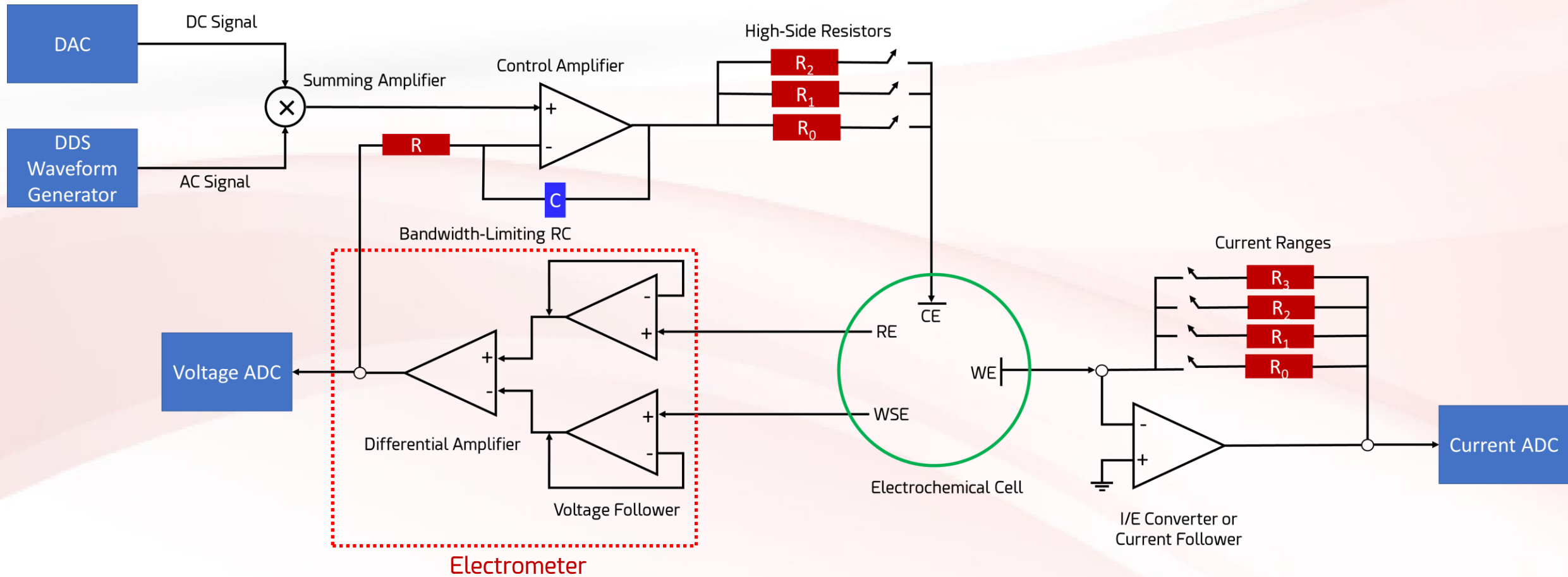

**DAC** = Digital to Analog Converter  
**ADC** = Analog to Digital Converter  
**DDS** = Direct Digital Synthesizer


# Simplified Galvanostat Design

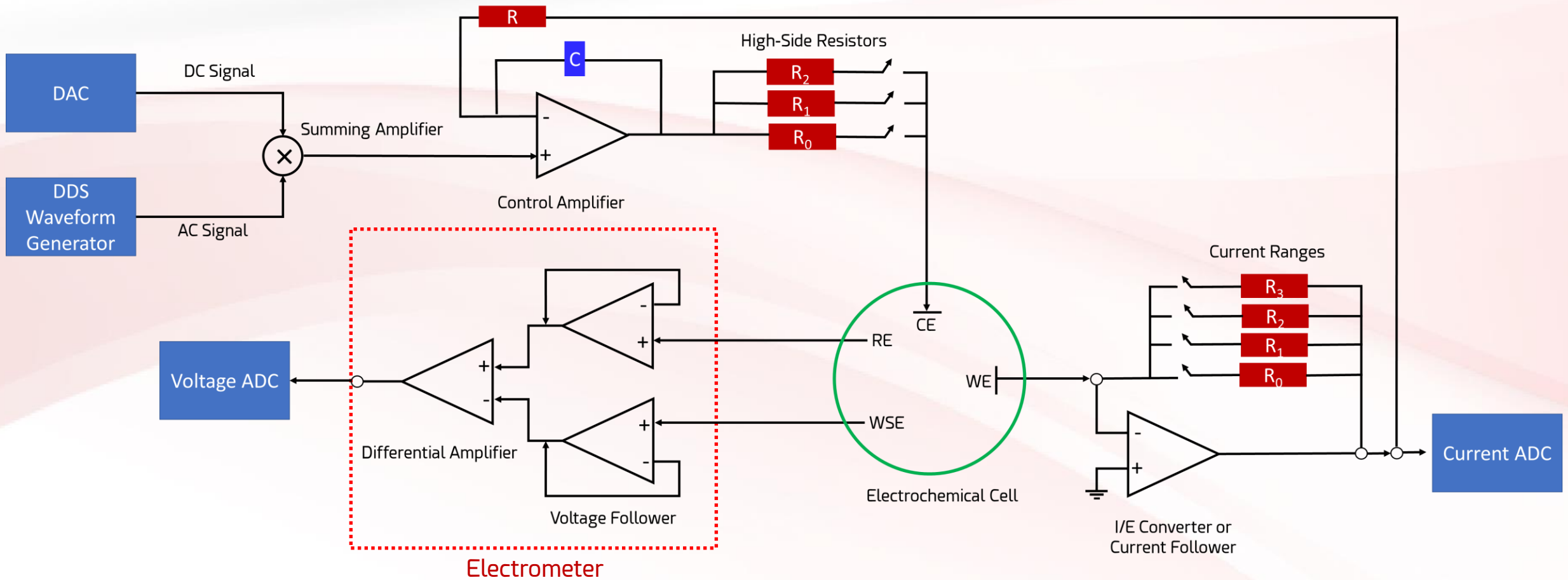



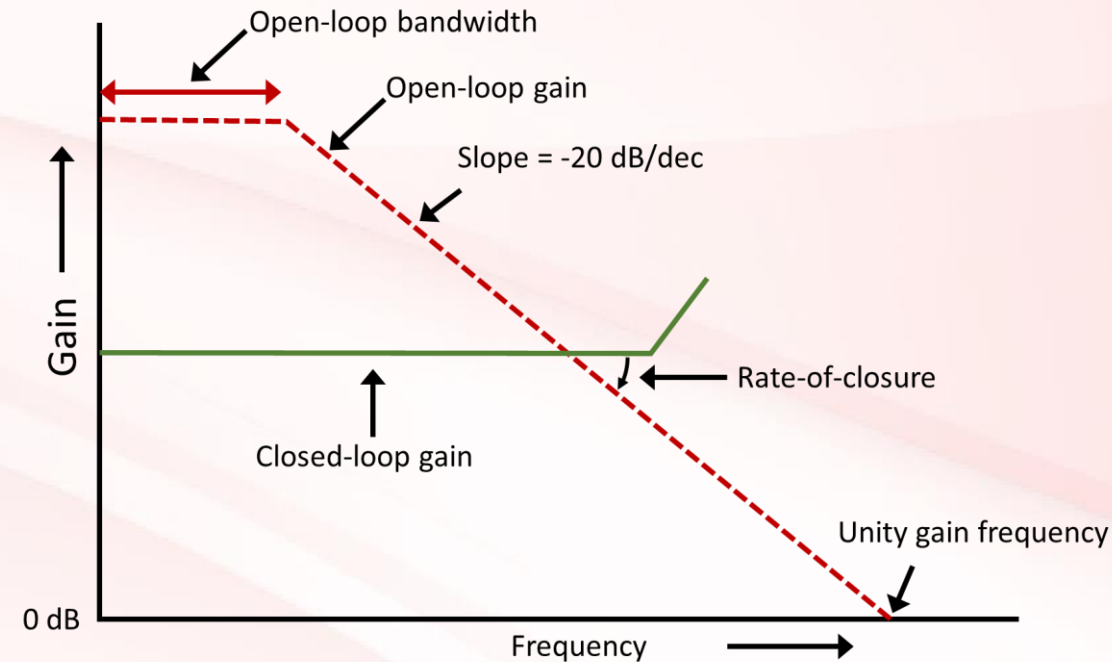
# Open-Loop Gain vs Closed-Loop Gain

- The gain of real op-amp is frequency dependent
- Closed-loop amplifier circuit cannot supply more gain at higher frequencies than available
  - Closed-loop is when a feedback loop exists
- The angle between closed-loop gain and open-loop gain is called the rate-of-closure, which determines stability of the circuit




# Stability Criteria


- The rate-of-closure determines if the circuit will be stable or not

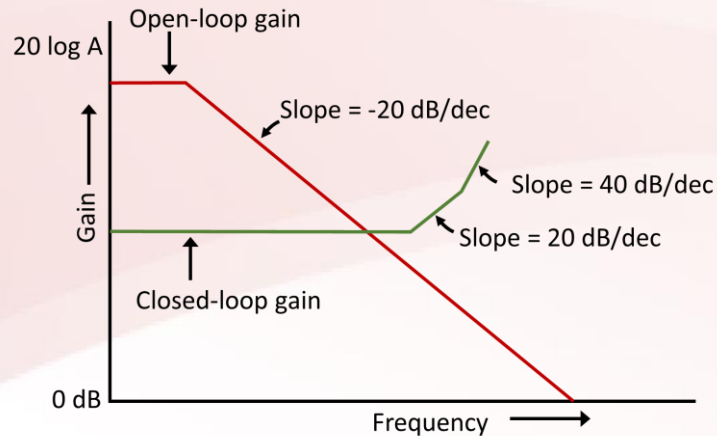

**Condition 1: Optimal stability**  
Rate-of-Closure < 40 DB

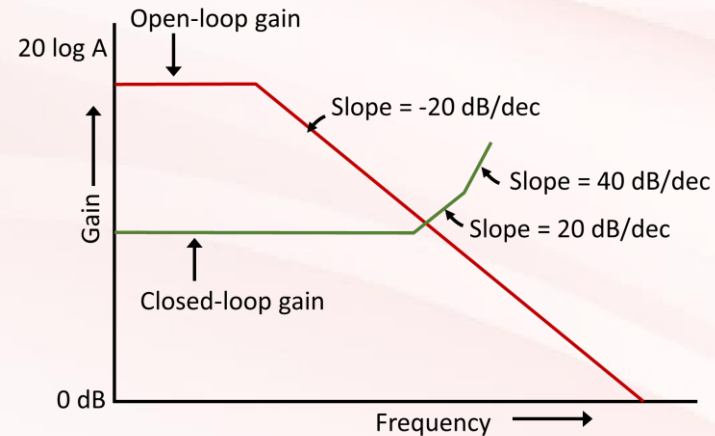

**Condition 2: Marginal stability**  
Rate-of-Closure = 40 DB


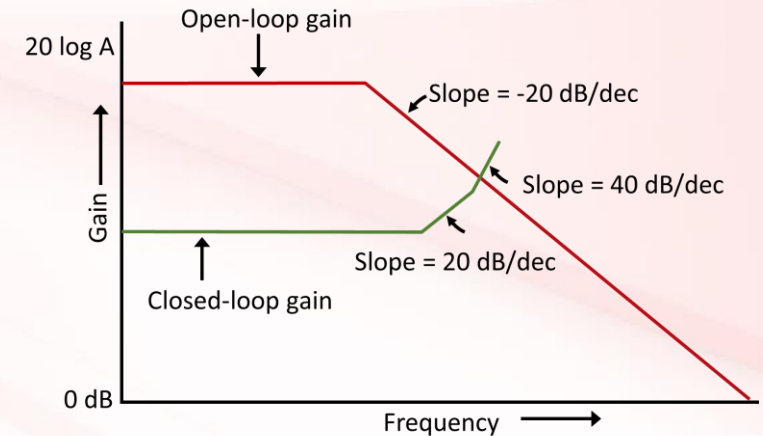


**Condition 3: Instability**  
Rate-of-Closure > 40 DB

- Rate-of-closure can be controlled by modulating the bandwidth of the control amplifier

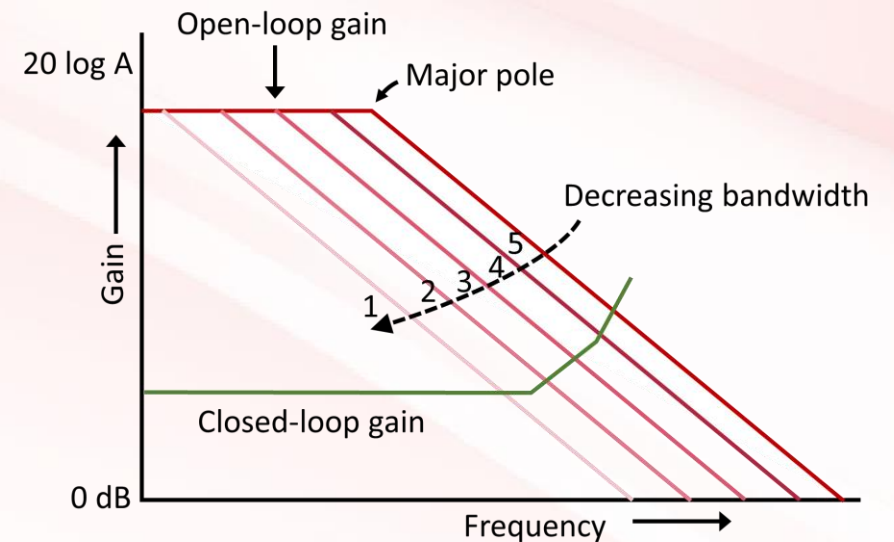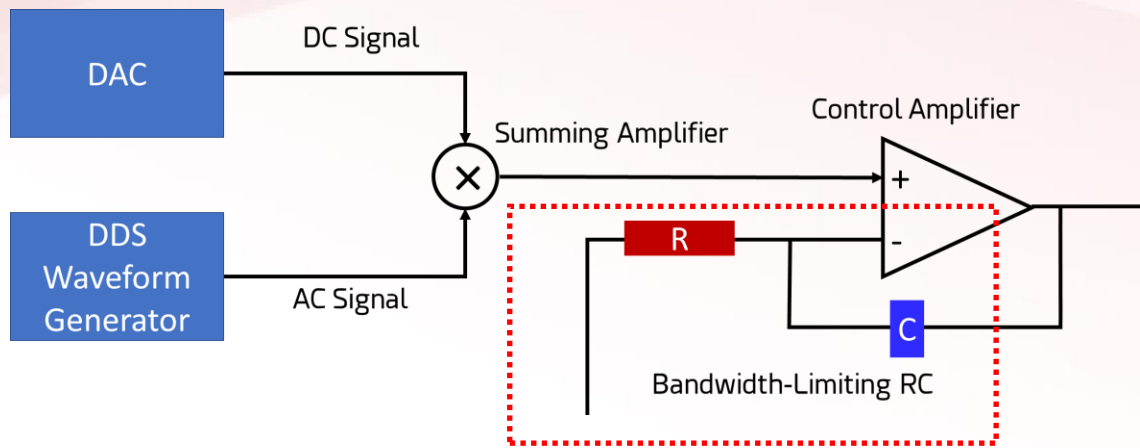
# Potentiostat Stability: *Bandwidth Index*

- Potentiostat stability can be controlled by varying bandwidth-limiting RC
- This is labeled as ***Bandwidth Index*** in the Squidstat User Interface software



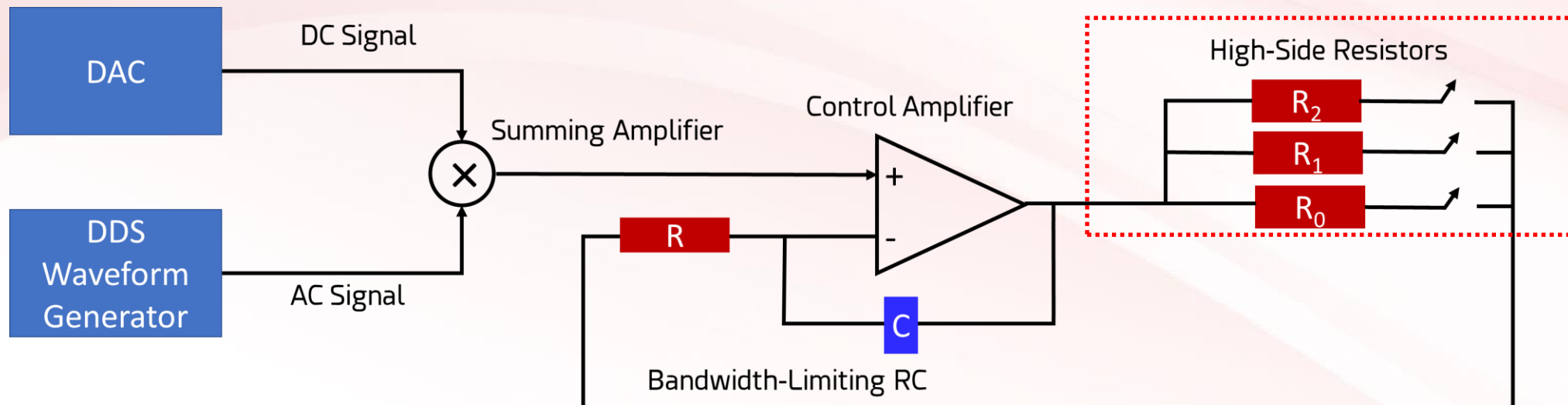
# Potentiostat Stability: *Stability Factor*

- The high-side resistors also control the bandwidth of the control amplifier, but do so in a less predictable way than the bandwidth-limiting RC



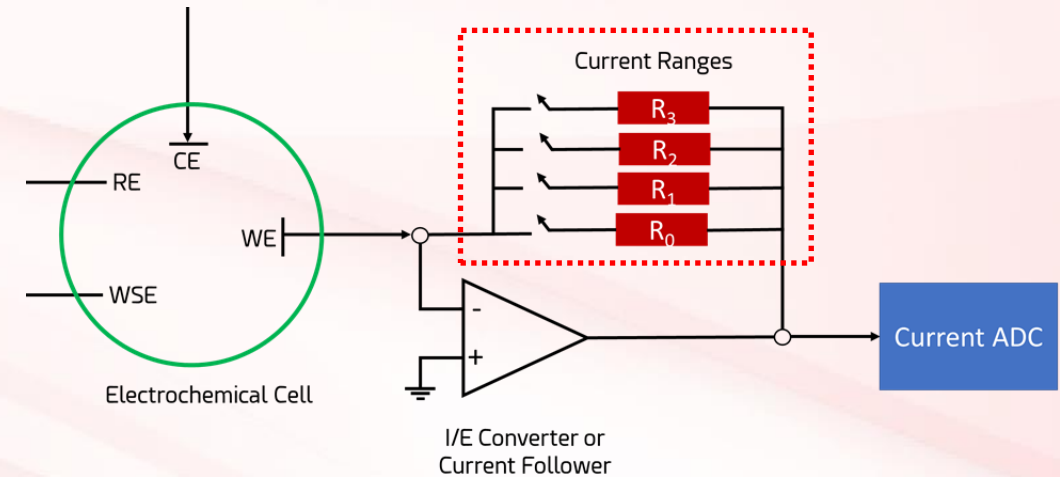
# Current Measurement

- In most potentiostats, current is measured by measuring the voltage drop across a resistor
  - $V_{out} = IR_x$ , where  $x = 0,1,2...N$
  - $N$  is the number of ranges
- If the max voltage drop across each resistor is 1 V...
  - For  $R = 10 \text{ Ohm}$ , Range = 0.1 A or 100 mA
  - For  $R = 100 \text{ Ohm}$ , Range = 0.01 A or 10 mA
- Resistor precision determines the current measurement accuracy
- Current ranging
  - Auto-range: the software/firmware selects the best resistor for accuracy
  - Fixed-range: the user selects the resistor



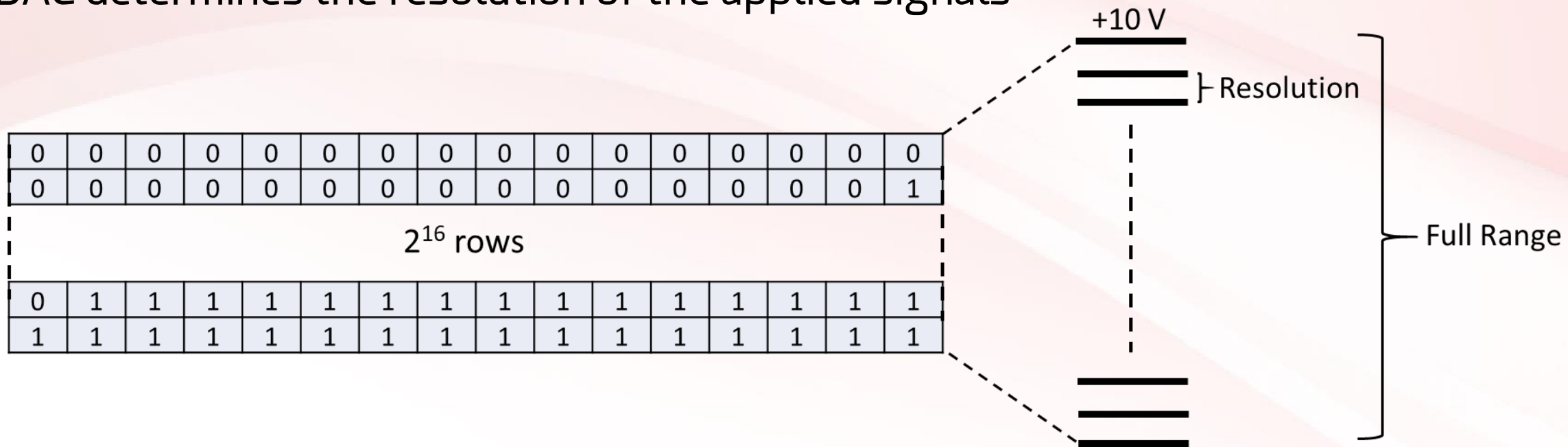
# Voltage and Current Ranges

- ADC determines the resolution of the measured signal
  - 16-bit ADC means there are  $2^{16}$  binary numbers to represent a voltage or current range
- DAC determines the resolution of the applied signals



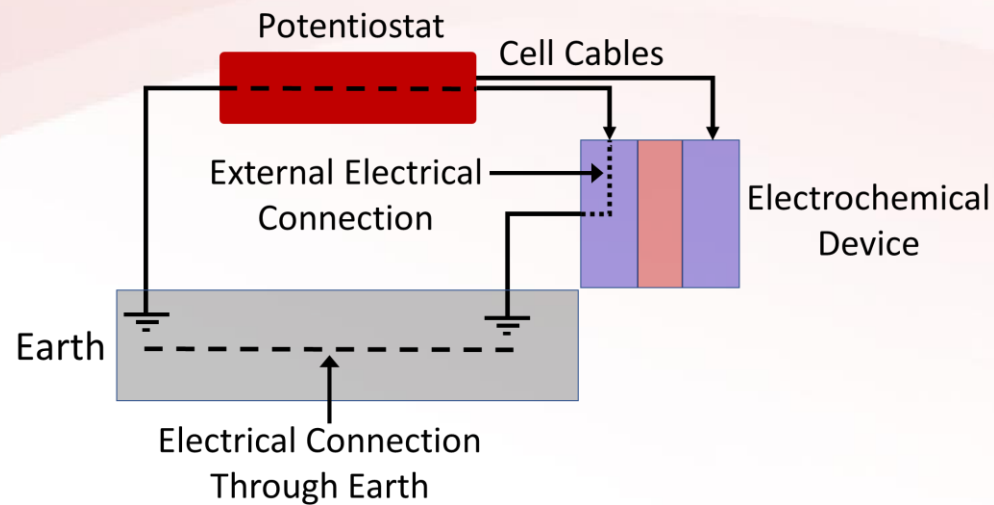
# Ground Loops

- "Ground" acts as a voltage reference point and current sink
- A ground loop occurs when two or more instrument are connected via "ground"
- A ground loop introduces noise and instability



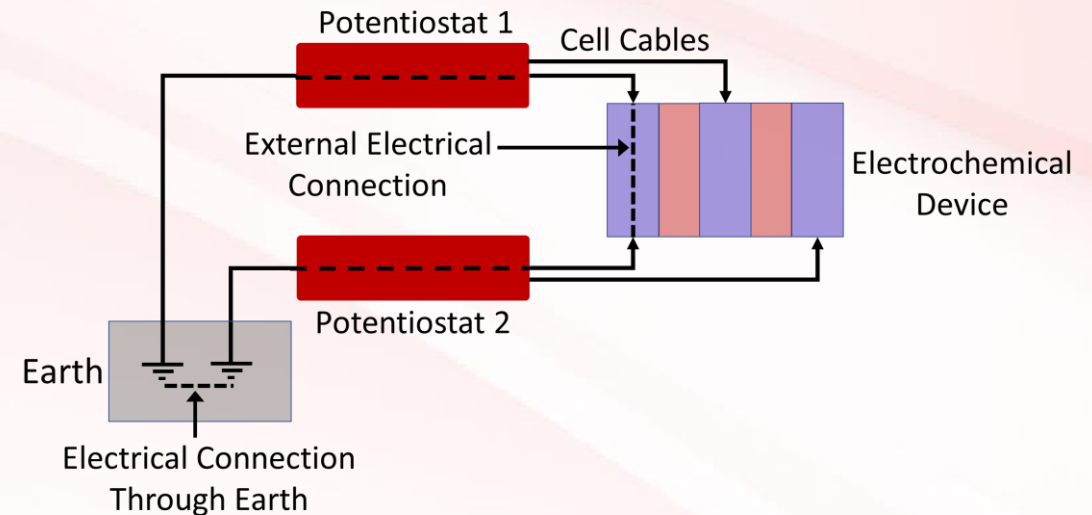**Ground Loop Through a Grounded Electrochemical Device**




**Two Potentiostats In Ground Loop Through Common Connection**



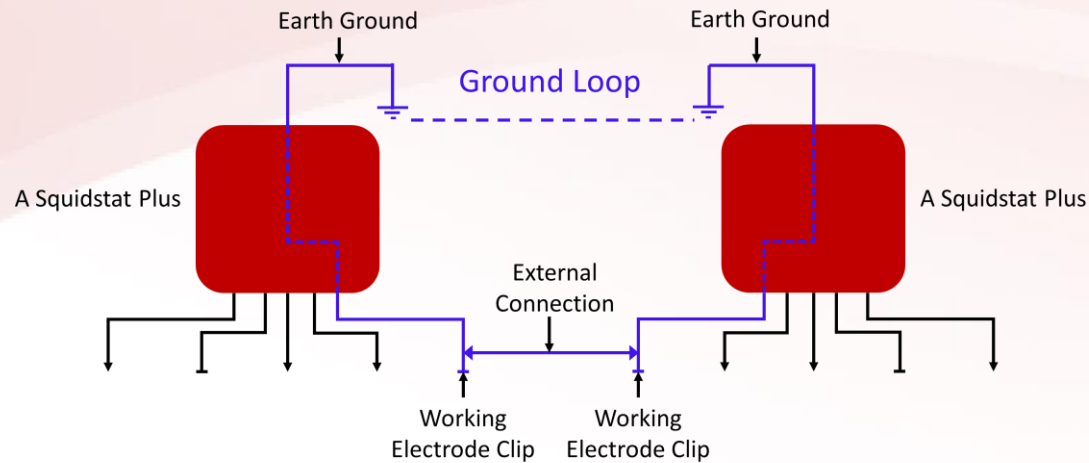
# Floating Mode

- When an instrument is disconnected from "Ground", it is in a floating mode



**Ground Mode**

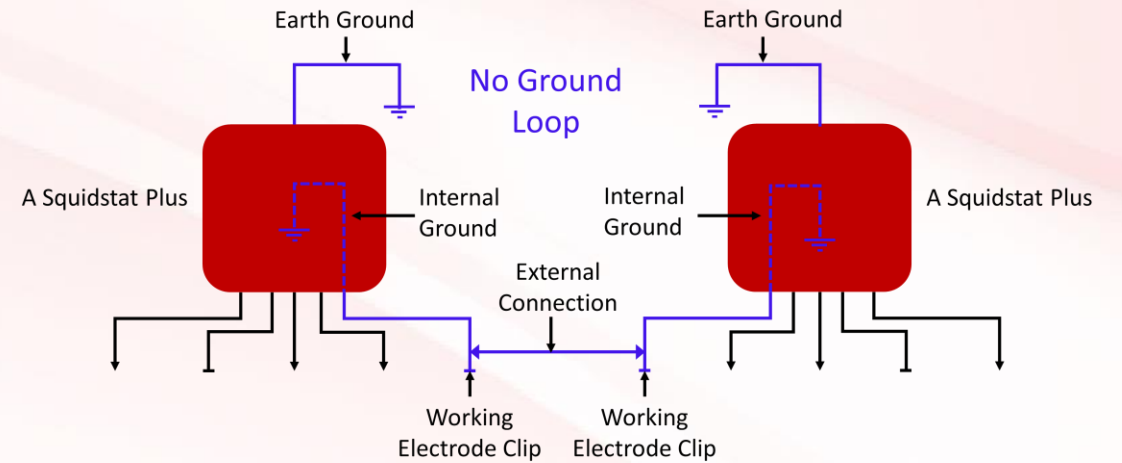

**Float Mode**


# Some Final Points to Consider

- Noise management
  - Thermal noise
  - Atmospheric noise
  - Shot noise
  - Flicker noise
  - Burst noise
  - Transit-time noise
  - Filter
- Issues caused by digital approximation of analog signals
- Data sampling
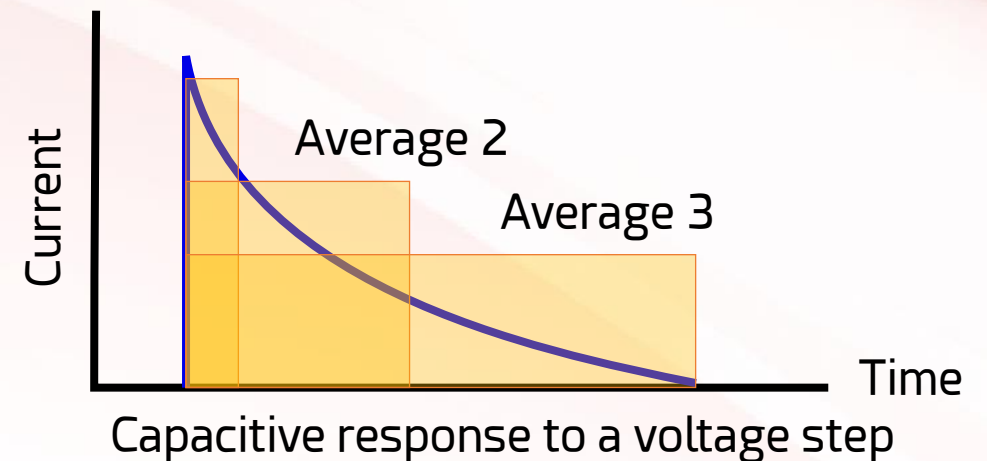
## Thermal Noise

$$E = (4 R k T \Delta F)$$

E is RMS noise in voltage  
R is resistance  
k is Boltzmann's constant  
T is temperature  
 $\Delta F$  is frequency range



FORWARD-THINKING HARDWARE. INTUITIVE SOFTWARE.

We're Devoted to Making Your Job **EASIER**



**Sujan Shrestha, PhD**

Applications Engineer

[sujan@admiralinstruments.com](mailto:sujan@admiralinstruments.com)

Office: +1 480 256 8706

Follow @potentiostats



[AdmiralInstruments.com](http://AdmiralInstruments.com)



*Making the next generation of electrochemistry instruments truly accessible worldwide*